

MILITARY COLLEGE OF SIGNALS
FINAL EXAM
BESE 16 – B
CE 230 Digital Logic Design

Instructor: Dr. Imran Siddiqi

Time: 2.5 hours
Max Marks: 50

FUNCTION IMPLEMENTATION

(6)

Question # 1

Given the Boolean function:

$$F(A, B, C, D) = \sum (0, 4, 8, 9, 10, 11, 12, 14)$$

Using 4 variable k-map, simplify and implement the above function using the following two-level forms:


- i. AND-OR-INVERT
- ii. OR-AND-INVERT
- iii. NOR-NOR

COMBINATIONAL LOGIC

(5+2+4)

Question # 2

 - a. Design a combinational circuit with three inputs a, b, c and three output x, y, z such that the output is 1's complement of the input. Simplify the Boolean expressions for x, y and z and show the circuit design.
- b. What is the output ($S_4S_3S_2S_1S_0$) of the following circuit?



- c. A combinational circuit is defined by the following functions:

$$F1(x, y, z) = xy' + x'z$$

$$F2(x, y, z) = \sum (0, 4, 6)$$

$$F3(x, y, z) = \prod (0, 4, 6)$$

- Implement the circuit using a decoder and external gates.
- Which external gates will you need if the decoder you are using is constructed with NAND gates?

(4+4)

Question # 3

- a. A 4x1 multiplexer has inputs x and y connected to the select lines S_1 and S_0 respectively. The data inputs I_0 to I_3 are as follows:
 $I_0=z$; $I_1=z'$; $I_2=0$; $I_3=1$


Find the Boolean function $F(x, y, z)$ that the multiplexer implements.

- b. Implement the full adder using two 8x1 MUXes. Connect x, y and C_{in} to the selection lines and 1 or 0 to the data lines.

(3+3)


Question # 4

 - a. Consider the following circuit with two decoders and one MUX.



- What is the output F if the select input $s = 0$.
- What is the output F if the select input $s = 1$.
- Write the Boolean expression for F in terms of A, B, C, X, Y, Z and s . s could be either 0 or 1.

 - b. For the given circuit show the truth table for inputs A, B, C and output F.




SEQUENTIAL LOGIC

(6+4+2)

 
Question # 5

- Design a sequential circuit that detects the pattern '0010' in a string of bits coming through an input line.
- It is required to design a state machine that outputs a '0' if an even number of 1's have been received and outputs a '1' otherwise. This can be achieved with the Mealy machine shown below:




Convert it into Moore machine and show the state tables for both the machines.

 - Assuming that the flip flop given below is initially cleared, what is the output Y if the serial input 0110 is applied to X.



Question # 6

- a. Consider the following latch.

 

Show the characteristic table for this latch. The table should include the following:

Clk	A	B	Q(t+1)
...
...

- b. Reduce the number of states in the following state table. Starting at state 'a' what is the output sequence if the input sequence 1001 is applied to the original state table before reduction.

Present state	Next State		Output	
	x=0	x=1	x=0	x=1
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	1	0
<i>c</i>	<i>f</i>	<i>e</i>	0	1
<i>d</i>	<i>g</i>	<i>a</i>	1	1
<i>e</i>	<i>d</i>	<i>e</i>	0	1
<i>f</i>	<i>g</i>	<i>a</i>	1	1

+++++++ Bon Courage ++++++