


Note: Attempt all questions. Be specific and to the point. All questions carry equal marks. Draw neat and clean diagrams.

Question No-1


- a. Show diagrammatically the complete Diode model in Forward and Reverse bias (5)
- b. Draw Energy diagram which should explain the formation of PN Junction and depletion region at the instant of Junction formation and at equilibrium. (3)
- c. Enumerate and sketch the Transistor configuration (2)

Question No-2

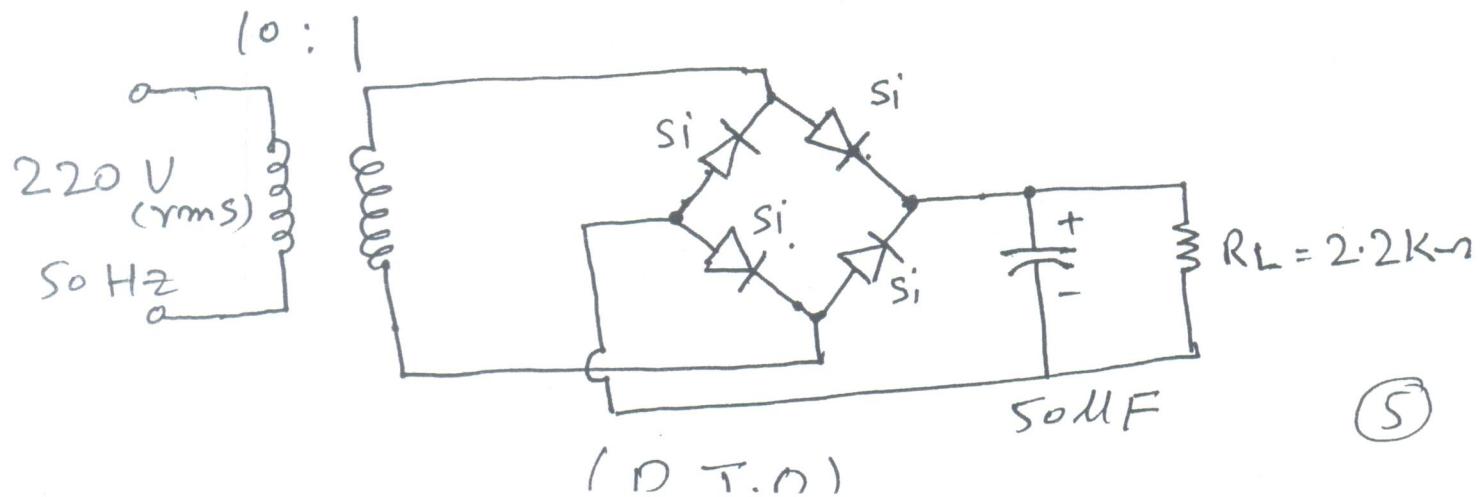- a. calculate ripple factor in the circuit



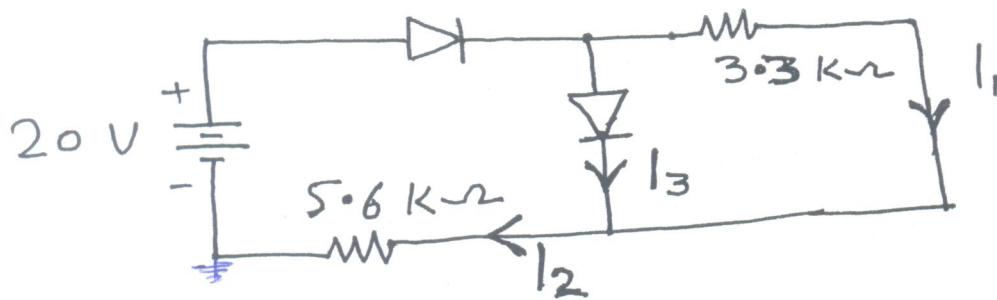
b. compute the value of I_1 , I_2 & I_3 in the network.
 Diodes are made up of Si material.



(5)

Question NO-3

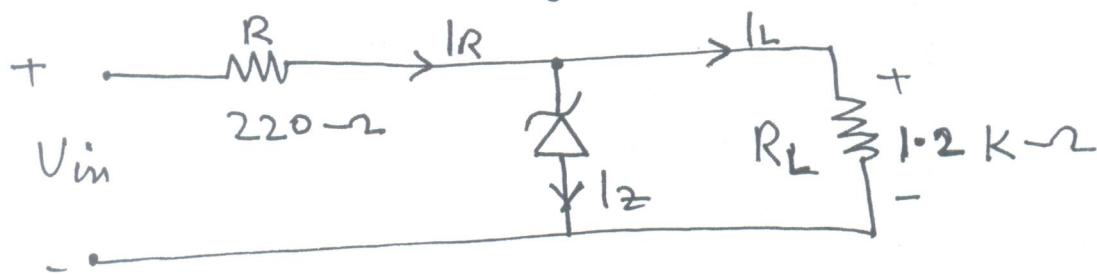a. calculate the range of values of V_{in} , that should maintain the zener diode in the 'ON' state. Zener voltage $V_z = 20V$ and $I_{z_m} = 60mA$



(6)

b. Differentiate between the followings.

i. LED and Photo diode

(2)

ii. Clipping and clamping action in diode.

(2)

(Good Luck).

MCS (Telecomm college)
Mid Term Exam (BESE 15A & B)


Solution:

Question No. 1

a. Complete Diode Model It consists of followings

- Barrier Potential
- Small Forward dynamic resistance (r_d)
- Large Internal reverse resistance (r_R). It provides path for reverse current.

Forward bias.

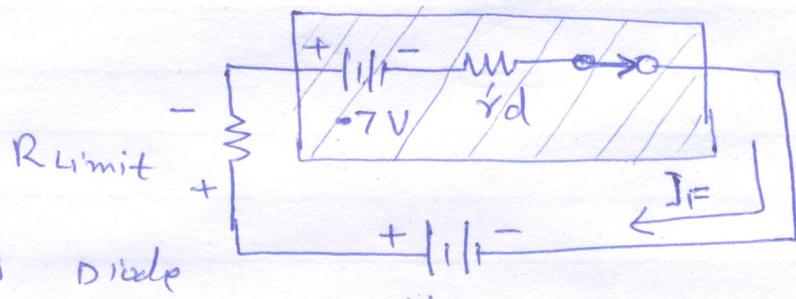

In forward bias diode act as closed switch


in series with barrier potential, r_d

(2)

Reverse bias

In reverse bias it act as an open switch

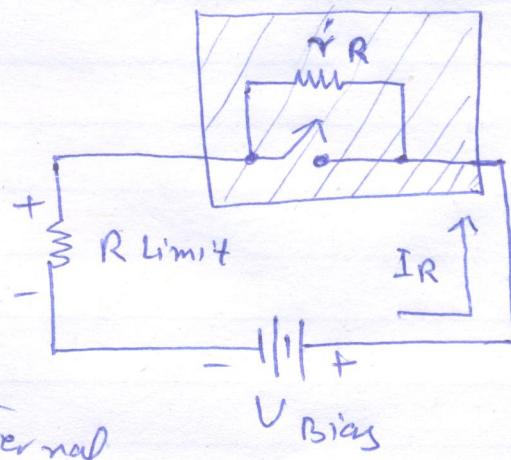in parallel with Large internal reverse resistance (r_R)




(2)

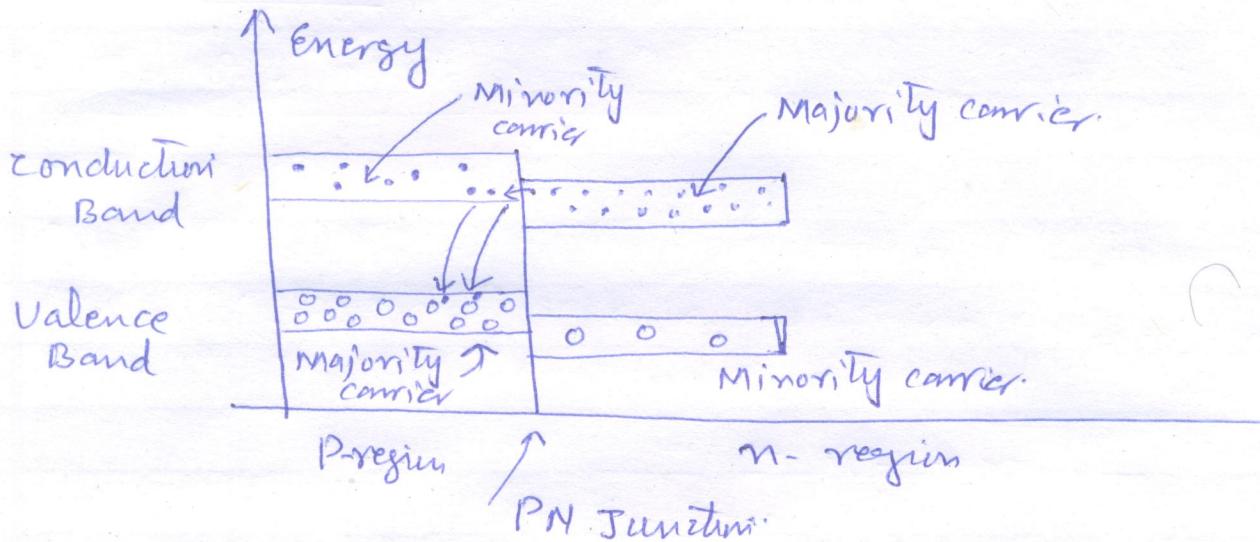(2)

- Due to atomic characteristics (3rd & 5th) group impurity atoms, the valence and conduction band in N-type are at a little bit lower energy level than P-type.

- The energy diagram at the instant of junction formation is as under-




There is overlapping in energy level, the electron in n-region occupy upper part of conduction band and easily diffuse across the junction. After crossing the junction they lose energy and falls into the holes in P-region valence band. The diffusion continues and depletion region begins to form.

In Equilibrium: the depletion region is complete and diffusion ceased and energy hill is formed. The energy level in n-region shifted down and energy gap between valence & conduction ^{band} _{remains} ^{the} same.

Diagram is shown on next page.

(13)

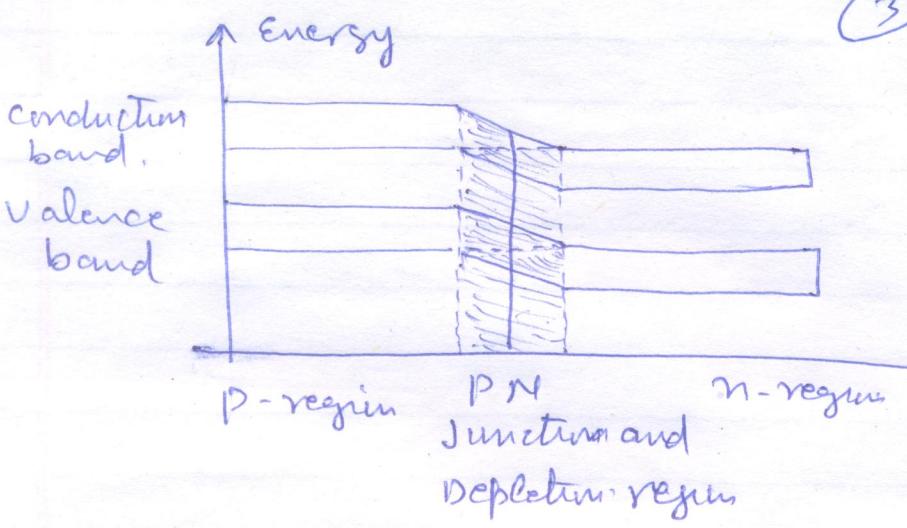

AT Equilibrium.

C. Configurations of BJT


② BJTs are used for amplification. There are 3 different configurations. In each arrangement one of the three leads is used as a common reference and other 2 are used as I/P and O/P connections.

The 3 circuit arrangements are:

* Common base.

nPN Transistor in

CB configuration

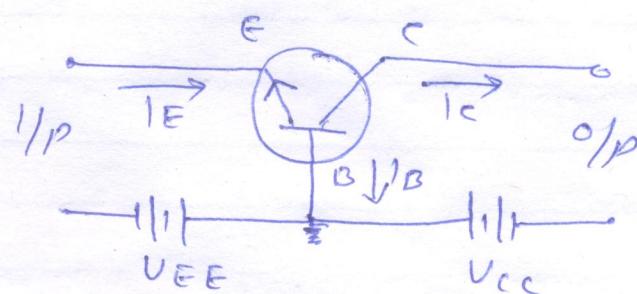


* Common Emitter configuration

nPN Transistor in
CE configuration

Common Collector config

nPN Transistor in

CC config.

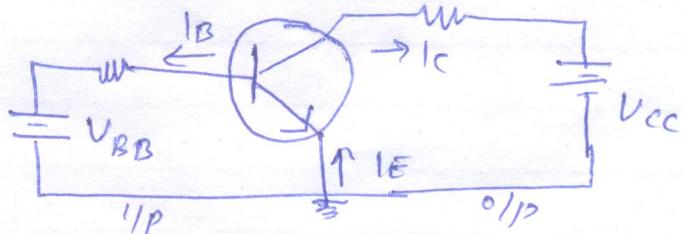


Question No. 2

(4)

a.

$$n = 0.1$$

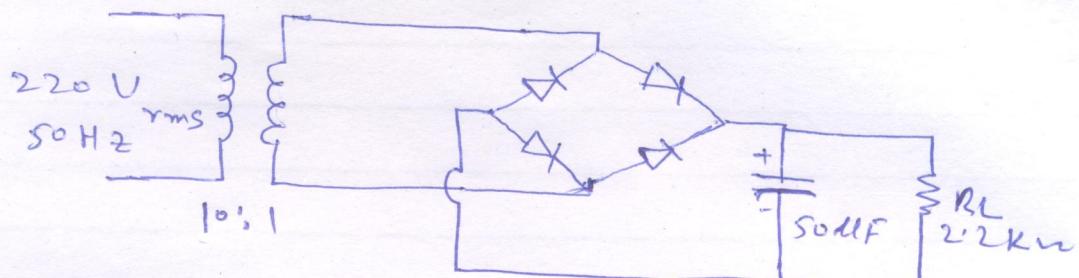

$$V_{P(\text{pri})} = 1.414 V_{\text{rms}} = 311.08 \text{ V}$$

$$V_{P(\text{sec})} = n V_{P(\text{pri})} = 0.1 (311.08) = 31.108 \text{ V}$$

Full wave rectified voltage

$$V_{P(\text{rect})} = V_{P(\text{sec})} - 1.4 \text{ V} = 29.708 \text{ V}$$

Freq of FWR voltage is $2 \times f_{ui} = 100 \text{ Hz}$

$$\begin{aligned} V_{r(pp)} &= \left(\frac{1}{f R_L C} \right) V_{P(\text{rect})} \\ &= \left(\frac{1}{(100 \text{ Hz})(2.2 \times 10^3 \Omega)(50 \times 10^{-6} \text{ F})} \right) 29.708 \text{ V} \\ &= (0.0909090) 29.708 = \boxed{2.70072} \end{aligned}$$

$$\begin{aligned} V_{DC} &= \left(1 - \frac{1}{2 f R_L C} \right) V_{P(\text{rect})} = \\ &= \left(1 - \frac{1}{(200)(2.2 \text{ k}\Omega)(50 \mu\text{F})} \right) 29.708 \\ &= (1 - 0.04545) 29.708 \\ &= (0.954545) 29.708 = \boxed{28.357636 \text{ V}} \end{aligned}$$


$\gamma_{\text{filter}} = \frac{V_{r(pp)}}{V_{DC}}$

$= \frac{2.70072}{28.357636}$

$= 0.09523783$

or
0.0952

b.

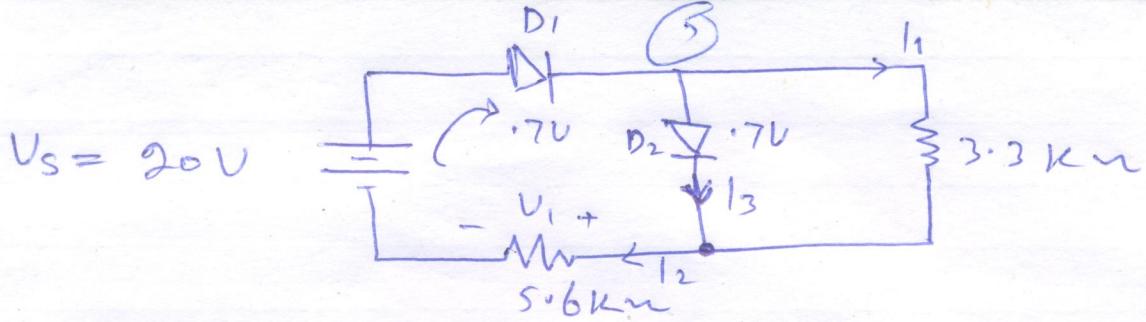

This is simple DC series parallel network.

$$I_1 = \frac{V_{D2}}{3.3\text{k}\Omega} = \frac{0.7\text{V}}{3.3\text{k}\Omega} = 0.212\text{ mA}$$

Apply KVL on Left loop.

$$-V_S + V_{D1} + V_{D2} + V_1 = 0$$

$$-20 + 0.7 + 0.7 = -V_1 \quad \text{or} \quad V_1 = 18.6\text{V}$$


$$I_2 = \frac{V_1}{5.6\text{k}\Omega} = \frac{18.6}{5.6\text{k}\Omega} = 3.32\text{ mA}$$

KCL at top or bottom node = $I_2 = I_1 + I_3$

$$I_3 = I_2 - I_1 = 3.11\text{ mA}$$

Question No. 3

a.

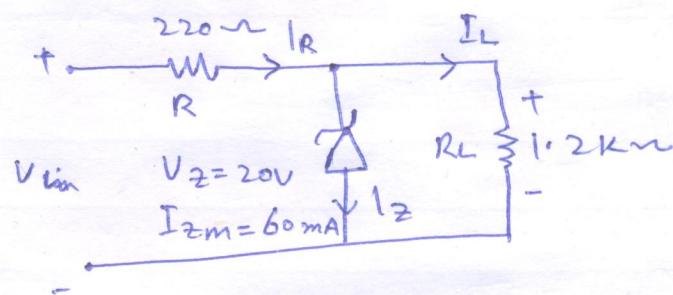

Inverse V. Division.

$$V_{in(\min)} = \frac{(R+R_L)}{R_L} V_Z = \frac{(220+1200)}{1200} 20\text{V} = 23.666 \cong 23.67\text{V}$$


$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20\text{V}}{1.2\text{k}\Omega} = 16.67\text{ mA}$$

$$I_R(\max) = I_{Zm} + I_L = 60\text{mA} + 16.67\text{mA} = 76.67\text{mA}$$

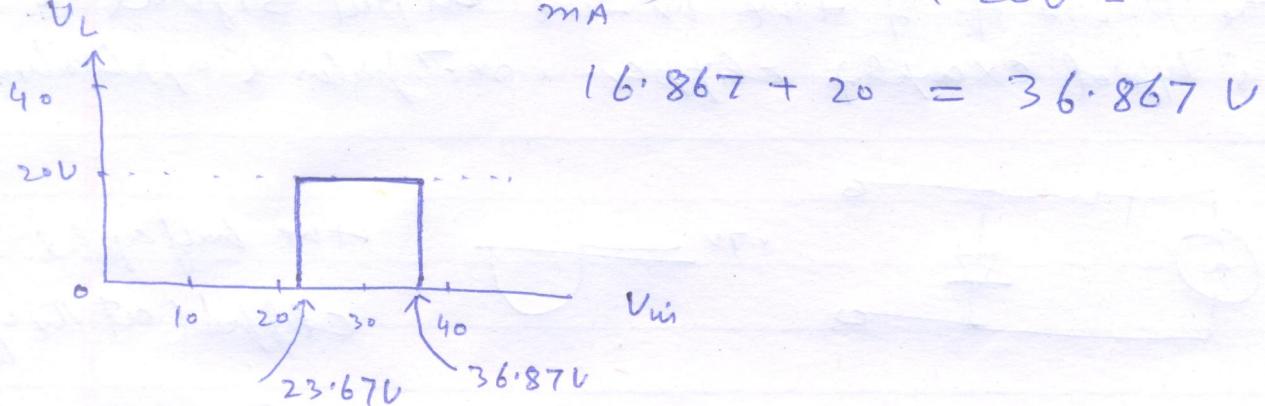(6)

$$V_{ui(max)} = I_{R(max)} \cdot R + V_2$$

$$(76.67) \frac{0.22 \text{ k} \Omega}{\text{mA}} + 20 \text{ V} = 36.87 \text{ V}$$



b. LED & Photo diode


(iv) In LED when device's forward bias electron cross PN junction form n-Type material and recombine with Holes in p-Type. the recombination of electron with hole release energy & light. The material permits the photons to be emitted as visible light. The wavelength depends on doping & determine the color of light. made up of GaAs, GaAsP or GaP. Si & Ge are not used as they produce heat. Required voltage are between 1.2 V to 3.2 V. Symbols:

Photo diode operates in reverse bias. It has small transparent window. when light strike on PN junction Reverse biased current flows and it increases with temp as more e, hole pair are generated. Value of current depends upon intensity of light. If no light no current flows. Symbols:


(7)

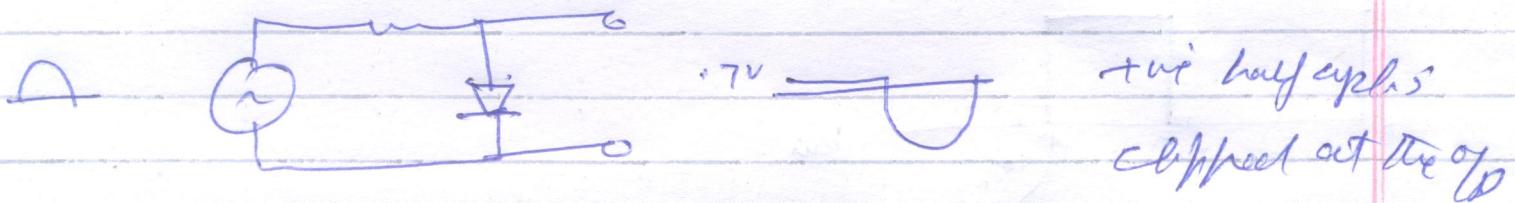ii) Clipping and clamping

clippers are also called limiter as they limit or clips the portion of the ac input signal
 Hw's typical example: clipper - rectifier's application



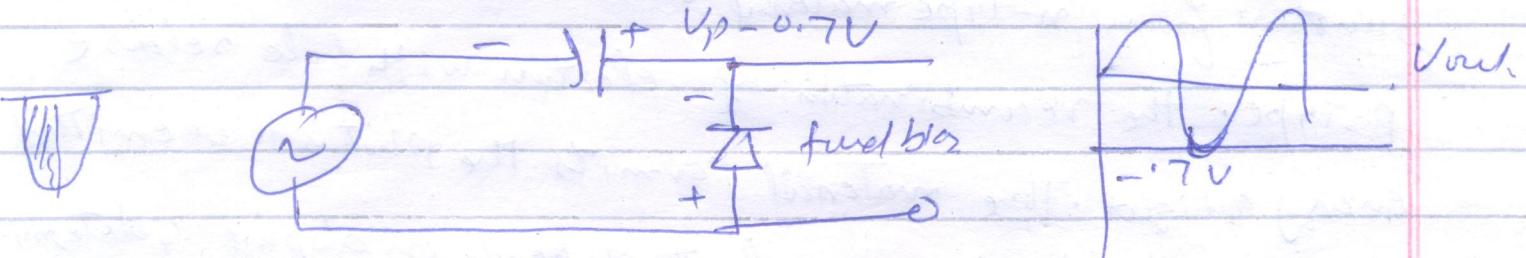- clamps are also called DC restorer. They insert +ve DC Level in the OP wave form. Capacitors used in place of resistors.



can be +ve or -ve clamps.

" " series or parallel " also
 typical uses: voltage multiplier.